

## CSE 4207 CT 4 Assignment

Roll No: 1903118

**Assignment Problem:** Combinational (ALU Op) + FSM Circuit using Verilog + Synthesis using 130nm Skywater PDK with OpenLane toolchain

**Category:** C

**Word Size** = 5 Bits

**ALU Operations** = XOR & ROR

**Solution:**

<https://drive.google.com/file/d/1T-JGRSbyM76HUGAloZIkAshH8jjWYLEv/view?usp=sharing>

**Video:**

[https://drive.google.com/file/d/1AYszy3tefUZkbTqrNzXDf1Pht8vkVW\\_b/view?usp=sharing](https://drive.google.com/file/d/1AYszy3tefUZkbTqrNzXDf1Pht8vkVW_b/view?usp=sharing)

<b>Have you uploaded the video?</b>	YES
<b>Check List 1:</b> Have you explained the design using testbenches to prove that your circuit is working correctly and giving correct results?	YES
<b>Check List 2:</b> Have you shown full synthesis results showing all the required info including RTL Synthesis, RTL Floorplan, RTL Power Analysis, GDS and Heatmap (for details, see assignment template doc)?	YES
<b>NB: Failing to upload video will cause heavy point penalty (5-6 Marks)</b>	
<b>NB: Failing to add any required info will cause point penalty (1-2 Marks)</b>	

**HDL Code:**

<b>Check List:</b> Have you added all the modules written in verilog including ALU, ALU_OP1, ALU_OP2, CONTROLLER, TOP, TOP_TESTBENCH, ALU_TESTBENCH, CONTROLLER_TESTBENCH?	YES
<b>NB: Failing to add any required info will cause point penalty (1-2 Marks)</b>	

top.v

<pre>module top(     input wire clk, reset, start,     output wire [4:0] R,     output wire ZF);  wire [4:0] fsm_A, fsm_B; wire op;</pre>
---

```

FSM fsm(
    .clk(clk),
    .reset(reset),
    .start(start),
    .A(fsm_A),
    .B(fsm_B),
    .op(op));

ALU alu(
    .A(fsm_A),
    .B(fsm_B),
    .op(op),
    .R(R),
    .ZF(ZF));

endmodule

```

FSM.v

```

module FSM(
    input wire clk, reset, start,
    output reg [4:0] A,B,
    output reg op);

    reg [4:0] pstate, nstate;
    parameter [4:0] START = 5'b00000,
        ONE = 5'b00001,
        TWO = 5'b00010,
        THREE = 5'b00011,
        FINISH = 5'b00100;

    always @(*) begin : NSOL
        begin : NSL
            case(pstate)

                START : nstate = start ? ONE :
START;

                ONE : nstate = TWO;

                TWO : nstate = THREE;

                THREE : nstate = FINISH;

```

```

        FINISH : nstate = START;

        default : nstate = 5'bx;

    endcase

end

    begin : OL
    case(pstate)

        START : begin
            A = 5'b00000;
            B = 5'b00000;
            op = 1'bx;
        end

        ONE : begin
            A = 5'b01011;
            B = 5'b01011;
            op = 1'b0;
        end

        TWO : begin
            A = 5'b00010;
            B = 5'b00011;
            op = 1'b1;
        end

        THREE : begin
            A = 5'b01100;
            B = 5'b00010;
            op = 1'b1;
        end

        FINISH : begin
            A = 5'b00000;
            B = 5'b00000;
            op = 1'bx;

        end

        default : begin
            A = 5'bx;
            B = 5'bx;
            op = 1'bx;
        end
    end

```

```

                                endcase
                                end
                                end

                                always @(posedge clk or negedge reset) begin :
PSR
                                begin
                                    if(~reset) begin
                                        pstate <= START;
                                        end

                                    else begin
                                        pstate <= nstate;
                                    end
                                end
                                end
                                end

                                endmodule

```


### RTL Timing Diagram:

**Check List:** Have you added all the timing diagrams of  
ALU\_TESTBENCH, CONTROLLER\_TESTBENCH, TOP\_TESTBENCH?

YES

**NB:** Failing to add any required info will cause point penalty (1-2 Marks)

Top\_tb.v -> gtkwave

 

### RTL Synthesis (130nm Skywater PDK with OpenLane toolchain):

**Check List:** Have you added *RTL synthesis summary*, *RTL synthesized design figure* and *Standard cell usage in synthesized design*?

YES

**NB: Failing to add any required info will cause point penalty (1-2 Marks)**

### RTL synthesis summary

top.v -> stat.rpt

Metrics	Count
Number of wires:	18
Number of wire bits:	22
Number of public wires:	11
Number of public wire bits:	15
Number of ports:	5
Number of port bits:	9
Number of memories:	0
Number of memory bits:	0
Number of processes:	0
Number of cells:	19

### Breakdown of stat.rpt

=== top ===

Number of wires:	8
Number of wire bits:	20
Number of public wires:	8
Number of public wire bits:	20
Number of ports:	5
Number of port bits:	9
Number of memories:	0
Number of memory bits:	0
Number of processes:	0
Number of cells:	2
ALU	1
FSM	1

### === FSM ===

Number of wires:	43
Number of wire bits:	103
Number of public wires:	8
Number of public wire bits:	24
Number of ports:	6
Number of port bits:	14
Number of memories:	0
Number of memory bits:	0
Number of processes:	0
Number of cells:	26
\$adff	1
\$eq	15
\$logic_not	3
\$mux	1
\$not	2
\$pmux	4

### === ALU\_XOR ===

Number of wires:	4
Number of wire bits:	20
Number of public wires:	3
Number of public wire bits:	15
Number of ports:	3
Number of port bits:	15
Number of memories:	0
Number of memory bits:	0
Number of processes:	0
Number of cells:	1
\$xor	1

### === ALU\_ROR ===

Number of wires:	10
Number of wire bits:	34
Number of public wires:	3
Number of public wire bits:	15
Number of ports:	3
Number of port bits:	15
Number of memories:	0
Number of memory bits:	0
Number of processes:	0

Number of cells:	5
\$eq	4
\$pmux	1

=== ALU\_FLAG ===


Number of wires:	4
Number of wire bits:	8
Number of public wires:	2
Number of public wire bits:	6
Number of ports:	2
Number of port bits:	6
Number of memories:	0
Number of memory bits:	0
Number of processes:	0
Number of cells:	2
\$logic_not	1
\$mux	1

=== ALU ===


Number of wires:	16
Number of wire bits:	64
Number of public wires:	8
Number of public wire bits:	32
Number of ports:	5
Number of port bits:	17
Number of memories:	0
Number of memory bits:	0
Number of processes:	0
Number of cells:	5
\$mux	2
ALU_FLAG	1
ALU_ROR	1
ALU_XOR	1

## RTL synthesized design figure

### hierarchy.dot

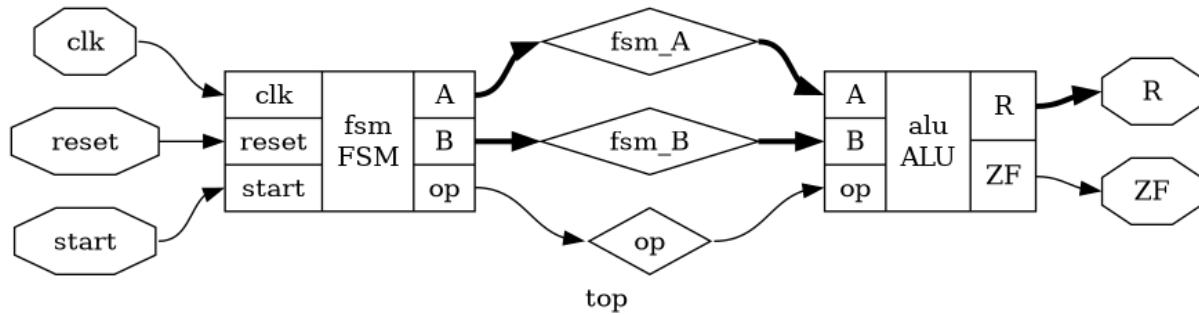

### primitive\_techmap.dot

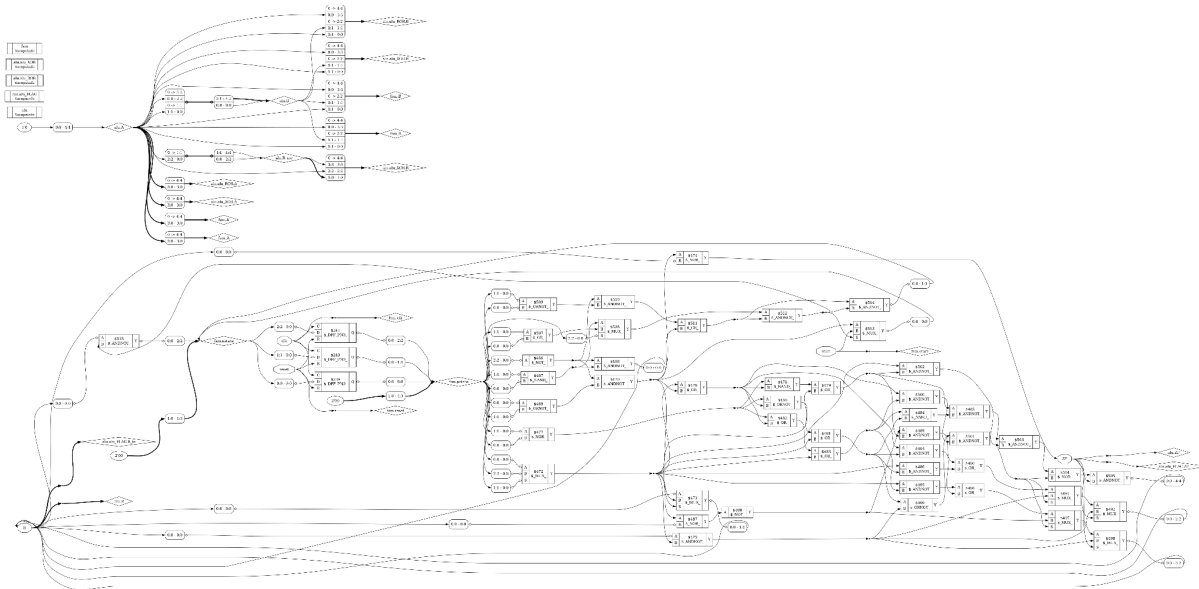

## Standard cell usage in the synthesized design

sky130_fd_sc_hd_and3_2	3
sky130_fd_sc_hd_buf_2	3
sky130_fd_sc_hd_conb_1	2
sky130_fd_sc_hd_dfrtp_2	3
sky130_fd_sc_hd_inv_12	1
sky130_fd_sc_hd_nand2_2	1
sky130_fd_sc_hd_nand2_4	1
sky130_fd_sc_hd_nor2_2	2
sky130_fd_sc_hd_o21a_4	1
sky130_fd_sc_hd_o221a_4	1
sky130_fd_sc_hd_xnor2_2	1



### RTL Floorplan (130nm Skywater PDK with OpenLane toolchain)

<b>Check List:</b> Have you added RTL Floorplan info?	YES
<b>NB: Failing to add any required info will cause point penalty (1-2 Marks)</b>	

[INFO] Extracting DIE\_AREA and CORE\_AREA from the floorplan

[INFO] Floorplanned on a die area of 0.0 0.0 50.0 50.0 (µm).

[INFO] Floorplanned on a core area of 5.52 10.88 44.16 38.08 (µm).

Writing metric design\_\_die\_\_bbox: 0.0 0.0 50.0 50.0

Writing metric design\_\_core\_\_bbox: 5.52 10.88 44.16 38.08

Setting global connections for newly added cells...

[INFO] Setting global connections...

Updating metrics...

Cell type report:	Count	Area (µm)
Buffer	3	15.01
Inverter	1	16.27
Sequential cell	3	<b>78.83</b>
Multi-Input combinational cell	12	<b>111.36</b>
Total	19	<b>221.46</b>

### RTL Power Analysis (130nm Skywater PDK with OpenLane toolchain)

<b>Check List:</b> Have you added RTL Power Analysis info?	YES
<b>NB: Failing to add any required info will cause point penalty (1-2 Marks)</b>	

```
=====
report_power
=====
===== nom_tt_025C_1v80 Corner =====
```


Group	Internal Power	Switching Power	Leakage Power	Total Power (Watts)	
Sequential	8.137030e-06	4.154676e-06	3.476829e-11	1.229174e-05	20.5%
Combinational	8.621550e-06	1.325401e-05	7.568256e-11	2.187564e-05	36.5%
Clock	2.200619e-05	3.840083e-06	1.711718e-10	2.584644e-05	43.1%
Macro	0.000000e+00	0.000000e+00	0.000000e+00	0.000000e+00	0.0%
Pad	0.000000e+00	0.000000e+00	0.000000e+00	0.000000e+00	0.0%
Total	3.876477e-05	2.124877e-05	2.816227e-10	6.001382e-05	100.0%
	64.6%	35.4%	0.0%		

## GDS Layout (130nm Skywater PDK with OpenLane toolchain)

**Check List:** Have you added the GDS Layout figure?

YES

 **NB:** Failing to add any required info will cause point penalty (1-2 Marks)



### Heatmap (130nm Skywater PDK with OpenLane toolchain)

Check List: Have you added the heatmap?	YES
NB: Failing to add any required info will cause point penalty (1-2 Marks)	

